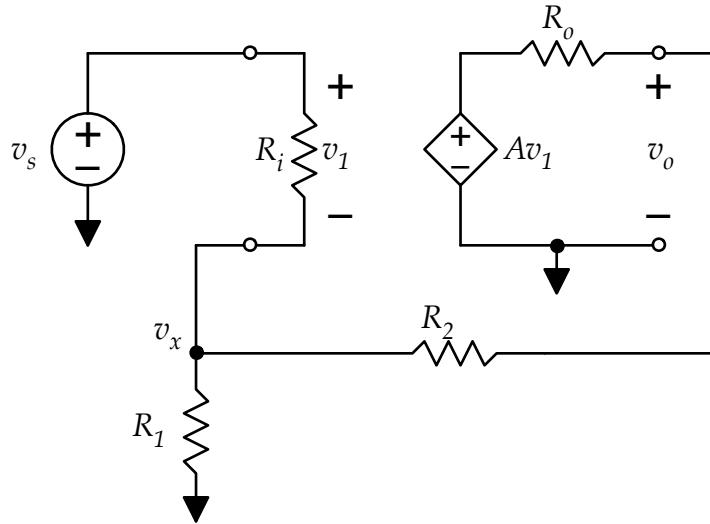


34. In the amplifier circuit below, the feedback network consists of the two resistors  $R_1 = 5 \text{ k}\Omega$ , and  $R_2 = 50 \text{ k}\Omega$ .




a. Start by letting the model be ideal:  $R_i \rightarrow \infty$ ,  $R_o \rightarrow 0$ , and  $A \rightarrow \infty$ . Calculate the closed-loop gain in that case.

$$G = v_o/v_s = \underline{\hspace{2cm}}$$

b. Then repeat with a model whose parameters are:  $R_i = 75 \text{ k}\Omega$ ,  $R_o = 250 \Omega$ , and  $A = 250$ . Note: Do not try to analyze this as a feedback problem. Just use circuit analysis to find the closed-loop gain. A couple of node equation might be one way to start. Recall that the notes had similar examples with either  $R_i < \infty$ , or  $R_o > 0$ , but not both at the same time.

$$G = v_o/v_s = \underline{\hspace{2cm}}$$

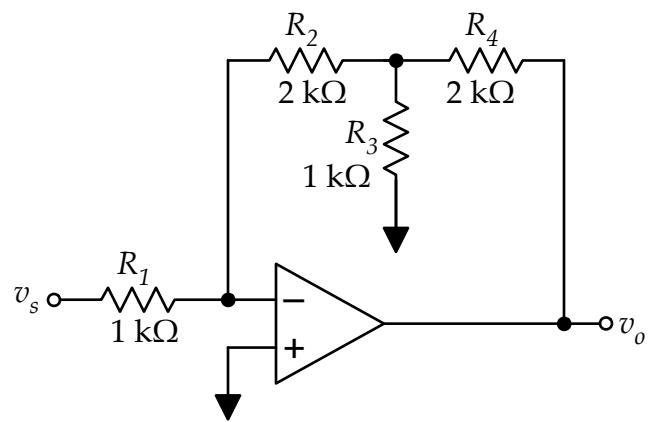35. Calculate the gain for the inverting-type circuit shown at right.




$$G = v_o/v_s = \underline{\hspace{10mm}}$$

36. Design a circuit using ideal op amps and resistors that takes three inputs,  $v_a$ ,  $v_b$ , and  $v_c$  and produces an output that is a weighted combination of the inputs:

$$v_o = -8v_a + 6v_b - 2v_c.$$

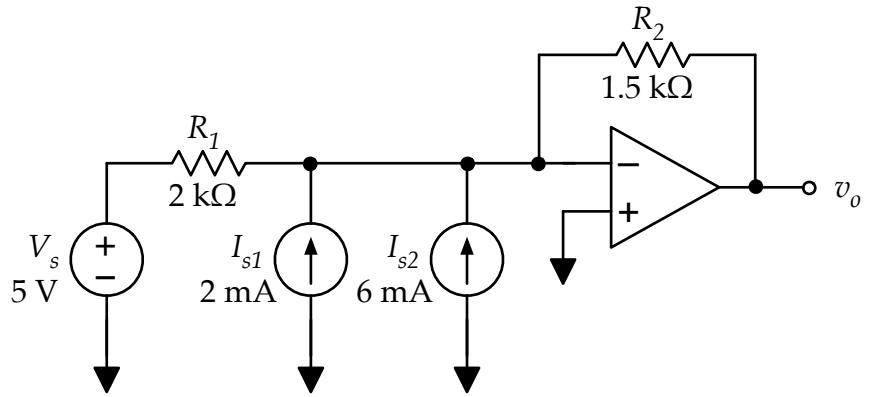37. Find the output voltage for the circuit shown.



$$v_o = \underline{\hspace{10mm}}$$


If the amplifier saturates at  $v_o = \pm 10$  V, calculate a new maximum value for  $I_{s2}$  so that output will not saturated.

38. Find the voltage  $v_{o1}$  and  $v_{o2}$  in the circuit at right.


Recall: For an op amp with a negative feedback loop,  $v_+ = v_-$ .

$$v_{o1} = \underline{\hspace{10mm}}$$

$$v_{o2} = \underline{\hspace{10mm}}$$

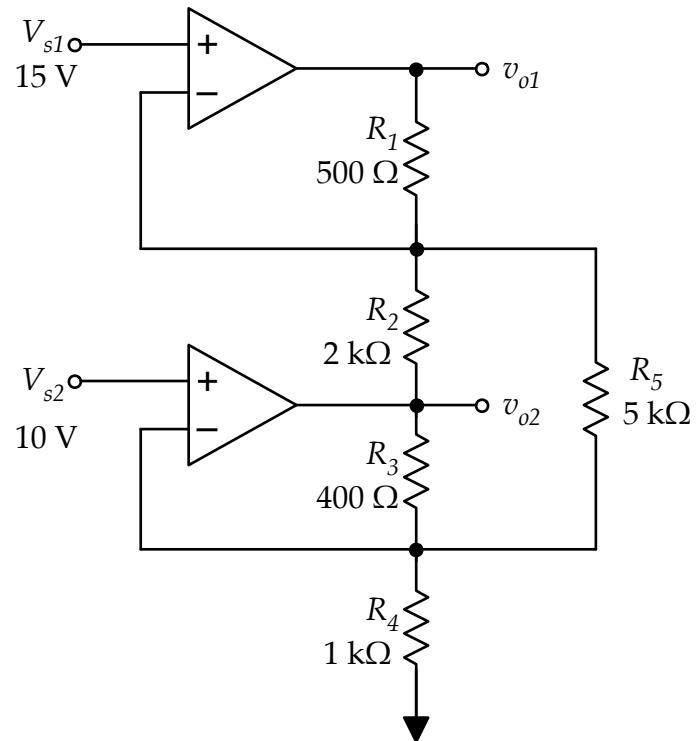

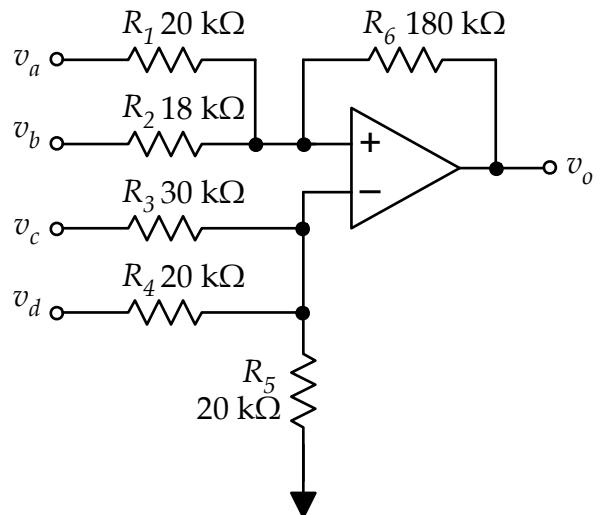39. The circuit at right might be called an “adder-subtracter”. Find an expression for the output voltage,  $v_o$ , in terms of the 4 input voltages,  $v_a$ ,  $v_b$ ,  $v_c$ , and  $v_d$ .



$$v_o = \underline{\hspace{100pt}}$$