

Answer the following questions:

1. For the oscillator in Figure 1:
 - a. Determine the oscillation frequency of the 555 astable oscillator.
 - b. To what value must C_{ext} be changed to achieve a frequency of 25 kHz?

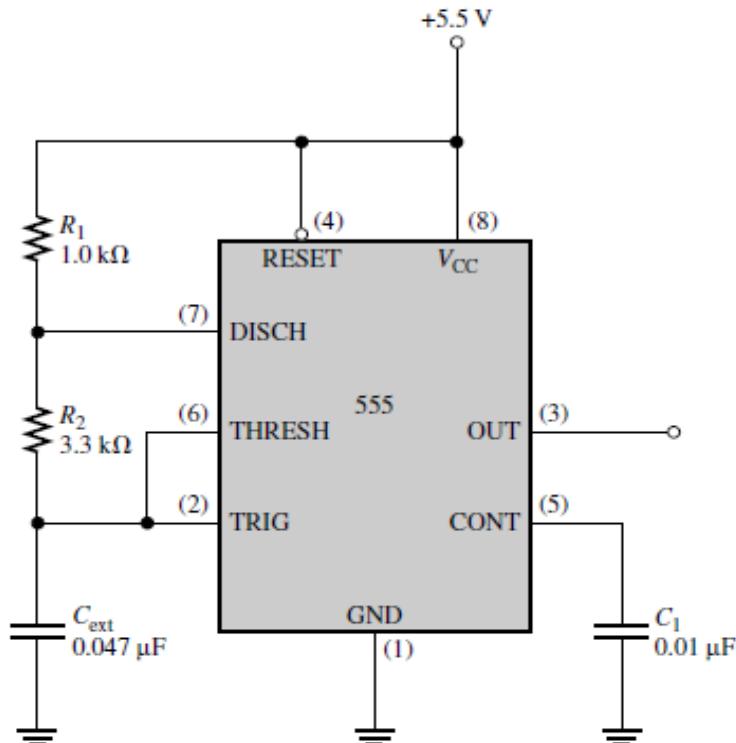


Figure 1

2. A 555 timer connected in the monostable configuration has a 56 kΩ external resistor and a 0.22 μF external capacitor. What is the pulse width of the output?
3. The output pulse width of a certain 555 one-shot is 12 ms. If $C_{ext}=2.2 \Omega F$, what is R_{ext} ?
4. The nominal output voltage of a certain regulator is 8 V. The output changes by 2 mV when the input voltage reduces from 12 V to 18 V. Complete the following:
 - a. Determine the line regulation and express it as a percentage change.
 - b. Express the line regulation in %/V.

5. Label the functional blocks for the voltage regulator in Figure 2.

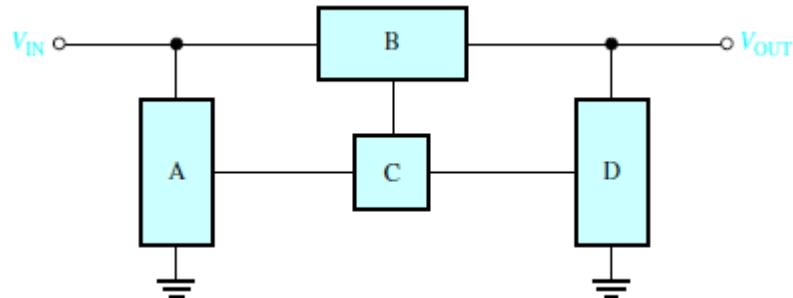


Figure 2

Block	Label
-------	-------

A	
---	--

B	
---	--

C	
---	--

D	
---	--

6. With reference to Figure 3, complete the following:

- Determine the output voltage for the series regulator.
- If R_3 is increased to 4.7 k Ω , what will happen to the output voltage?
- If the zener voltage is 2.7 V instead of 2.4 V, what would be the output voltage?

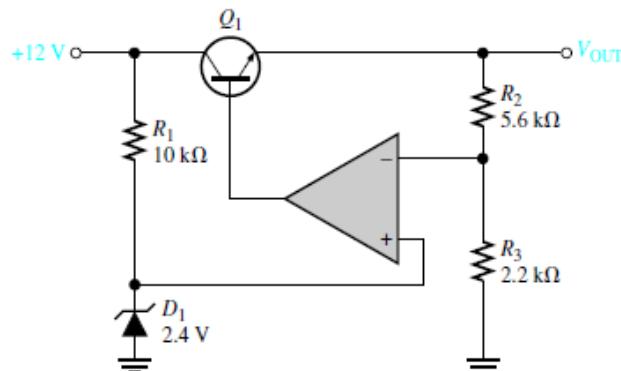


Figure 3

7. Using the shunt regulator in Figure 4, answer the following:

- When the current through R_L increases, does Q_1 conduct more or less? Explain.
- Assume the current through R_L remains constant and V_{IN} changes by 1 V. What is the change in the collector current of Q_1 ?

c. With a constant input voltage of 17 V, the load resistance is varied from $1.0 \text{ k}\Omega$ to $1.2 \text{ k}\Omega$.

Neglecting any change in output voltage, how much does the shunt current through Q_1 change?

d. Assume the maximum allowable input voltage is 25 V.

- What is the maximum possible output current when the output is short-circuited?
- What power rating should R_1 have?

e. In the regulator circuit, determine R_{ext} if the maximum internal regulator current is to be 250 mA.

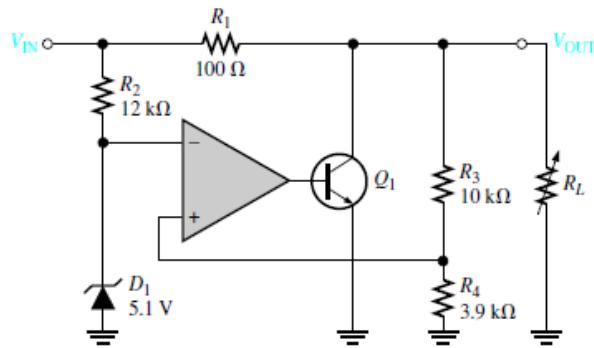


Figure 4

8. Using a 7812 voltage regulator and a 10Ω load in Figure 5, how much power will the external pass transistor have to dissipate? (The maximum internal regulator current is set at 500 mA by R_{ext})

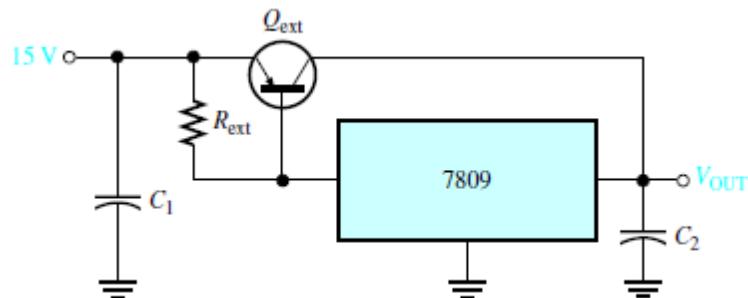


Figure 5

Submission Requirements:

Submit the completed exercise containing your responses to the instructor for evaluation.

Evaluation Criteria:

Your submission will be evaluated against the following criteria:

- Did you answer all questions correctly?
- Did you show work for all the calculations?